 


Lab 9: Flip-flops and Counter

Objective: To implement a RS latch and a binary counter with D-type flip flops.

Provided: 74X374 (D flip-flops), 7400 (quad 2-input NAND), breadboard.

9.1 Experiment: RS Latch



S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table

Input $S=0$ $R=0$ is undesirable or forbidden because the output $Q=1$ $Q_{\text{prime}}=1$ is an invalid state.

9.2 Experiment: Binary Counter

Present State				Next State				Unused
$Q_4(t)$	$Q_3(t)$	$Q_2(t)$	$Q_1(t)$	D_4 $Q_4(t+1)$	D_3 $Q_3(t+1)$	D_2 $Q_2(t+1)$	D_1 $Q_1(t+1)$	
0	0	0	0	0	0	0	1	1010
0	0	0	1	0	0	1	0	1011
0	0	1	0	0	0	1	1	1100
0	0	1	1	0	1	0	0	1101
0	1	0	0	0	1	0	1	1110
0	1	0	1	0	1	1	0	1111
0	1	1	0	0	1	1	1	Don't Care
0	1	1	1	1	0	0	0	
1	0	0	0	1	0	0	1	
1	0	0	1	0	0	0	0	

Q_4Q_3	Q_2Q_1
1	1
1	1
X	X
1	X

$$D_1 = Q_1'$$

Q_4Q_3	Q_2Q_1
1	1
1	1
X	X
	X

$$D_2 = Q_2Q_1' + Q_4'Q_2'Q_1$$

Q_4Q_3	Q_2Q_1
1	1
1	1
X	X
X	X

$$D_3 = Q_3Q_2' + Q_3Q_1' + Q_3'Q_2Q_1$$

Q_4Q_3	Q_2Q_1
1	1
1	1
X	X
1	X

$$D_4 = Q_4Q_1' + Q_3Q_2Q_1$$

Circuit Diagram:

