

## Lab 6: Build and analyze a circuit


## 1 Objective

In this experiment the student will build and analyze a simple circuit.


**Provided:** 1 7404 chip, 1 7408 chip, 1 7432 chip, breadboard.

## 2 Experiment

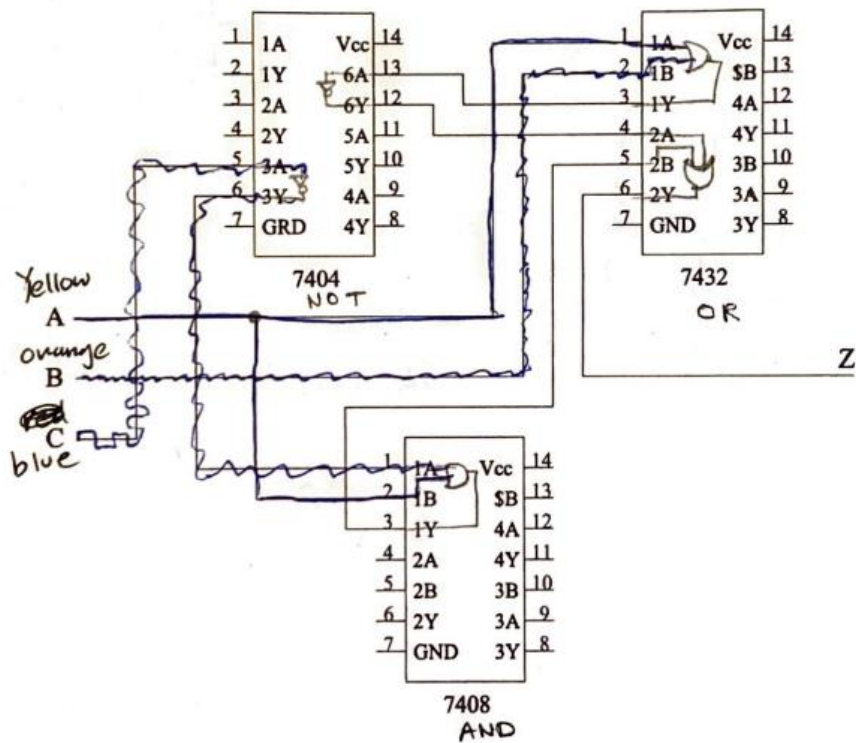
1. Build the following circuit using the specified IC's. Make sure you connect the Vcc and GND in each of the IC's appropriately. Note that A, B and C are the inputs and Z is the output.



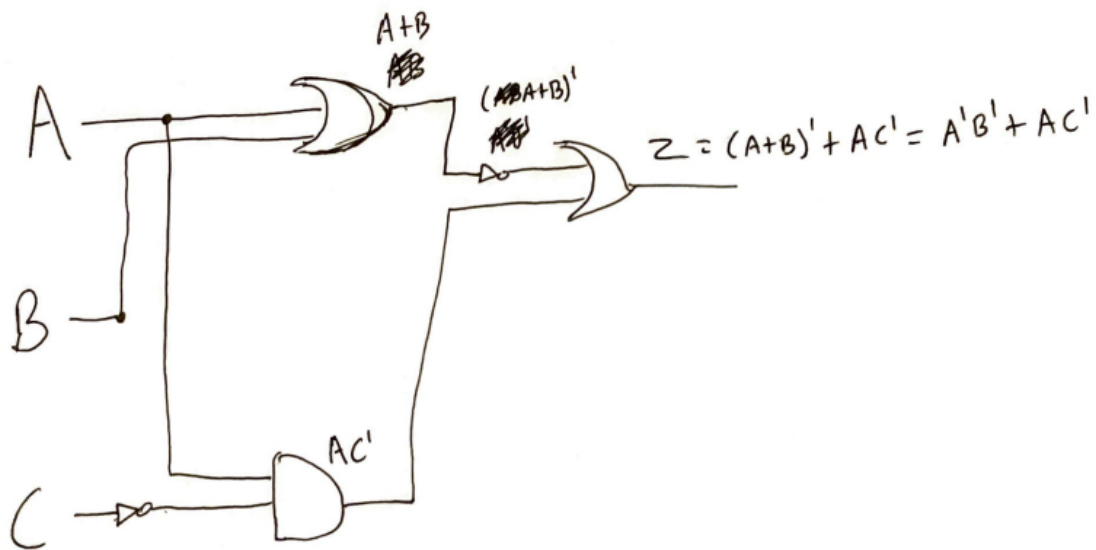2. By tracing the circuit find Z as a function in terms of A, B and C.
3. Simplify function Z. using K-map
4. Create the truth table for Z.
5. For each of the input combination in the circuit, verify that the corresponding value of Z agrees with that in the truth table.



K-map

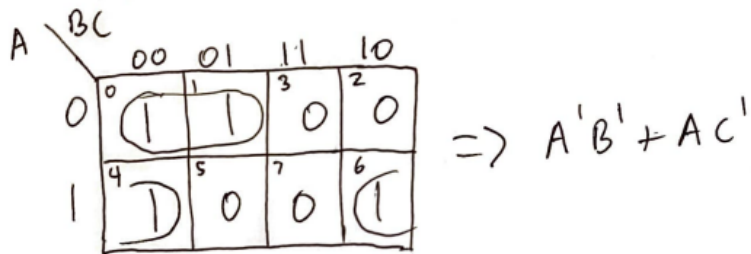

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Everything Checks Out.