


Daniel Delgado Acosta
Professor Duck Chung
CSE 4030
October 26th, 2022

Lab 9: AC Steady State Analysis

Introduction

In this lab, we have to find the voltage and current as a function of time across two circuits that consist of resistors, inductors, and capacitors . First, we show our work by hand then use Pspice simulation software to check. The purpose of this lab is to understand the instantaneous signal in ac circuits.

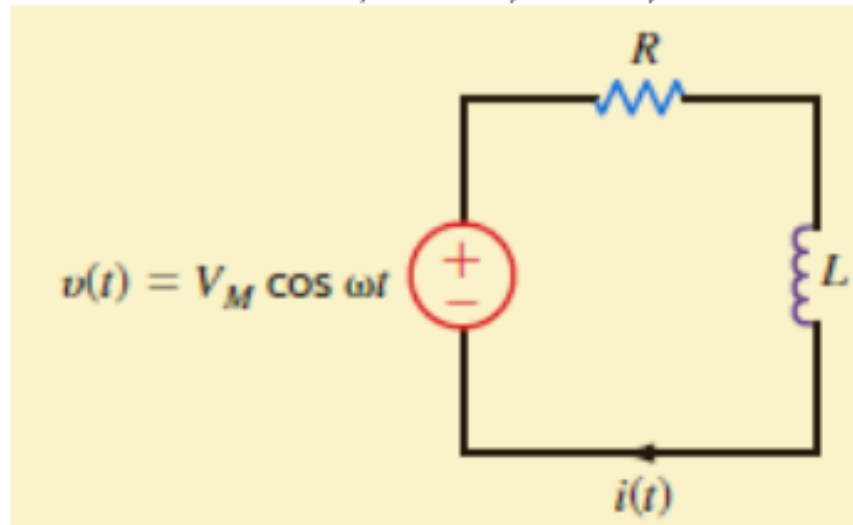
1-1 $V_M = 10\sqrt{2}V$, $f=60Hz$, $R= 2\Omega$, $L=5.3mH$



Preparation

1. Find $v(t)$, $v_L(t)$, $i(t)$. (.calculate by hand)
2. By using pspice simulation, find $v(t)$, $v_L(t)$, $i(t)$.

1-2 $V_S(t) = 24\cos(377t+60^\circ)$

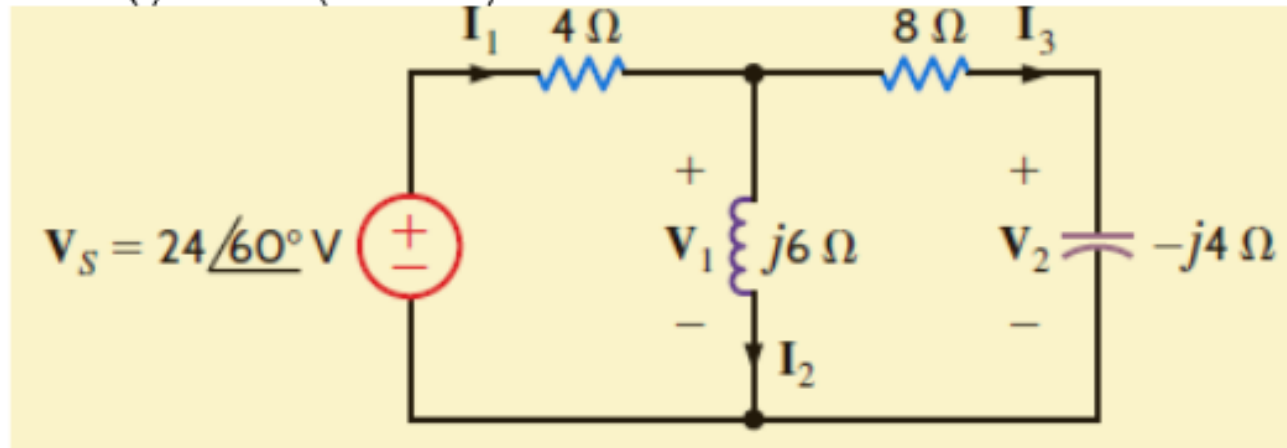

Preparation

1. Find I_1 , I_2 , and I_3 (calculate by hand),
2. By using pspice, find I_1 , I_2 , and I_3 .

Hand Written Work

Circuit 1:


$$V_m = 10\sqrt{2} \text{ V} \quad f = 60 \text{ Hz}$$

$$R = 2 \Omega \quad L = 5.3 \text{ mH}$$

$$v(t) = V_m \cos(\omega t)$$

$$f = \frac{\omega}{2\pi} \Rightarrow \omega = (60)2\pi$$

$$\omega = 377$$

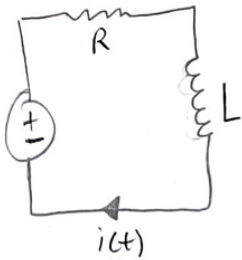

$$V_m \cos(\omega t) = L \frac{di(t)}{dt} + Ri(t)$$

$$i(t) = A \cos(\omega t + \phi)$$

$$\rightarrow i(t) = \frac{V_m}{\underbrace{\sqrt{R^2 + \omega^2 L^2}}_A} \cos(\omega t - \underbrace{\tan^{-1} \frac{\omega L}{R}}_{\phi})$$

$$e^{j\omega t} = \cos(\omega t) + j\sin(\omega t), \quad v(t) = V_m e^{j\omega t}, \quad I_m = A, \quad V_m = RI_m e^{j0} + j\omega LI_m e^{j0}$$

$$v(t) = 10\sqrt{2} \cos(377t) \text{ V}, \quad i(t) = \frac{10\sqrt{2}}{\sqrt{4 + 377^2 \cdot 5.3 \cdot 10^{-6}}} \cos\left(377t - \tan^{-1} \frac{377(5.3 \text{ mH})}{2}\right)$$


$$\rightarrow i(t) = 5 \cos(377t - 0.785) \text{ A} \quad V_s = V_R + V_L \Rightarrow V_L = V_s - V_R$$

Circuit 2:

$$\omega = 377$$

$$V_s = 24 \angle 60^\circ \text{ V}$$

$$V_s(t) = 24 \cos(377t + 60)$$

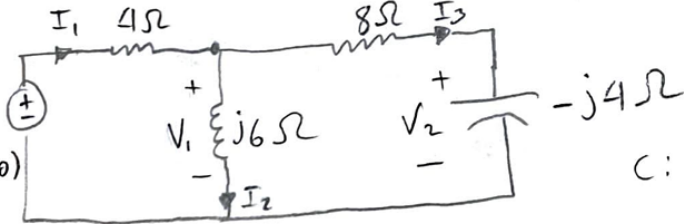

$$L: j\omega L = j6 \Rightarrow L = \frac{6}{377} = 0.016$$

$$C: \frac{-j}{\omega C} = -j4 \Rightarrow C = \frac{1}{377(4)} = 0.66 \text{ mF}$$

$$Z = 4 + \frac{(j6)(8 - j4)}{j6 + 8 - j4} = 4 + \frac{24 + j48}{8 + j2} = 4 + 4.24 + j4.94 = 9.61 \angle 30.94^\circ$$

$$I_1 = \frac{V_s}{Z} = \frac{24 \angle 60^\circ}{9.61 \angle 30.94^\circ} = 2.5 \angle 29.06^\circ \text{ A} \quad V_1 = V_s - 4I_1 = 16.26 \angle 78.43^\circ \text{ V}$$


$$I_2 = \frac{V_1}{j6} = \frac{16.26 \angle 78.43^\circ}{6 \angle 90^\circ} = 2.71 \angle -11.58^\circ \text{ A}$$

$$I_3 = \frac{V_1}{8 - j4} = 1.82 \angle 105^\circ \text{ A} \quad V_2 = I_3(-j4) = 7.28 \angle 15^\circ \text{ V}$$


Pspice simulation

Circuit 1:


Code used

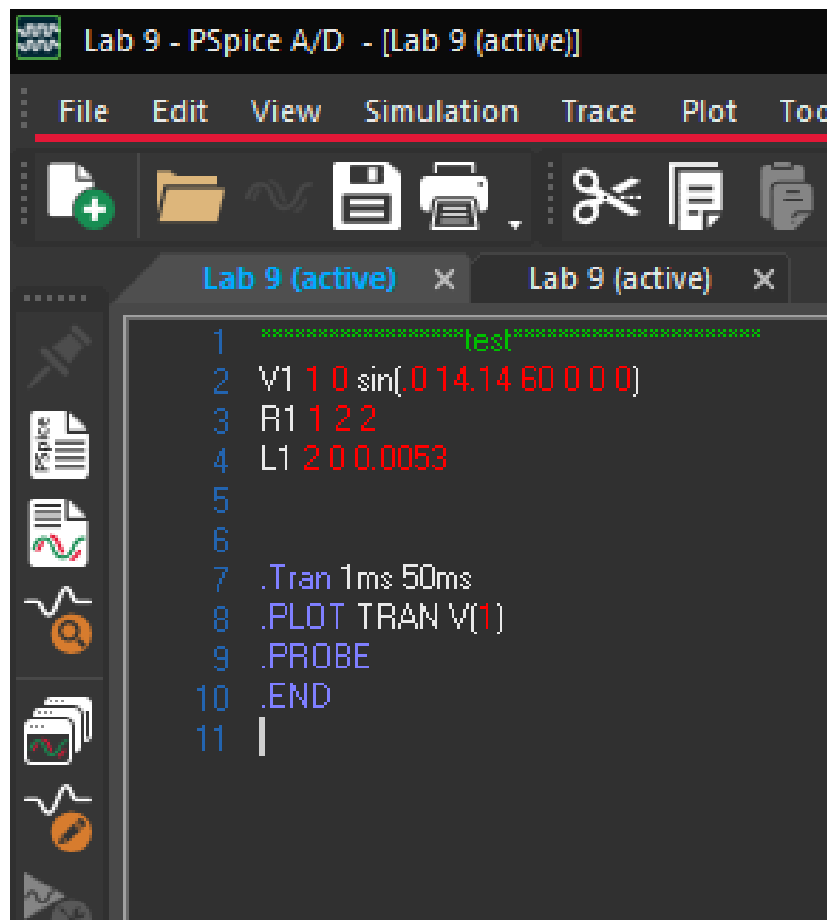


All traces

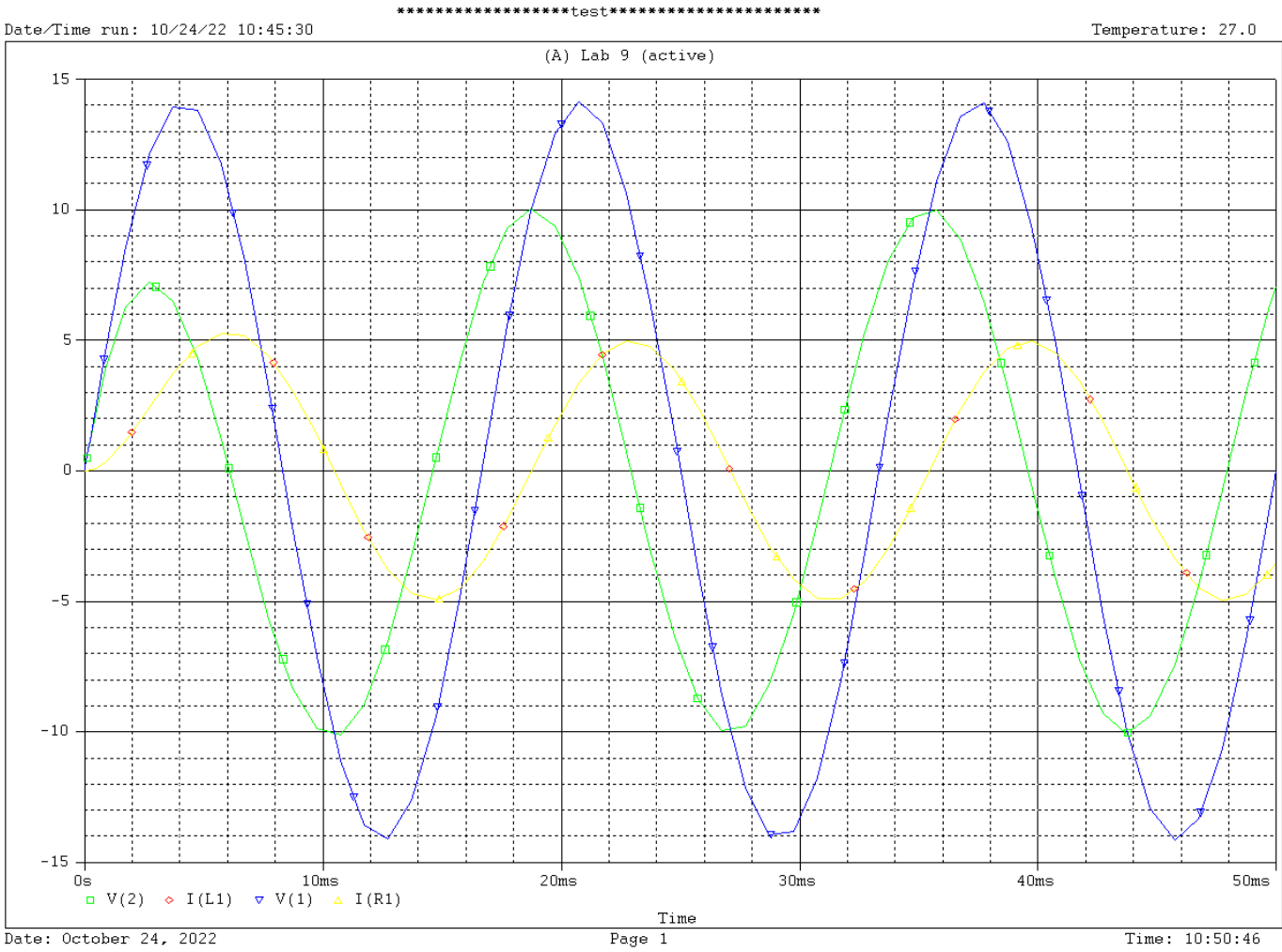

Voltage traces

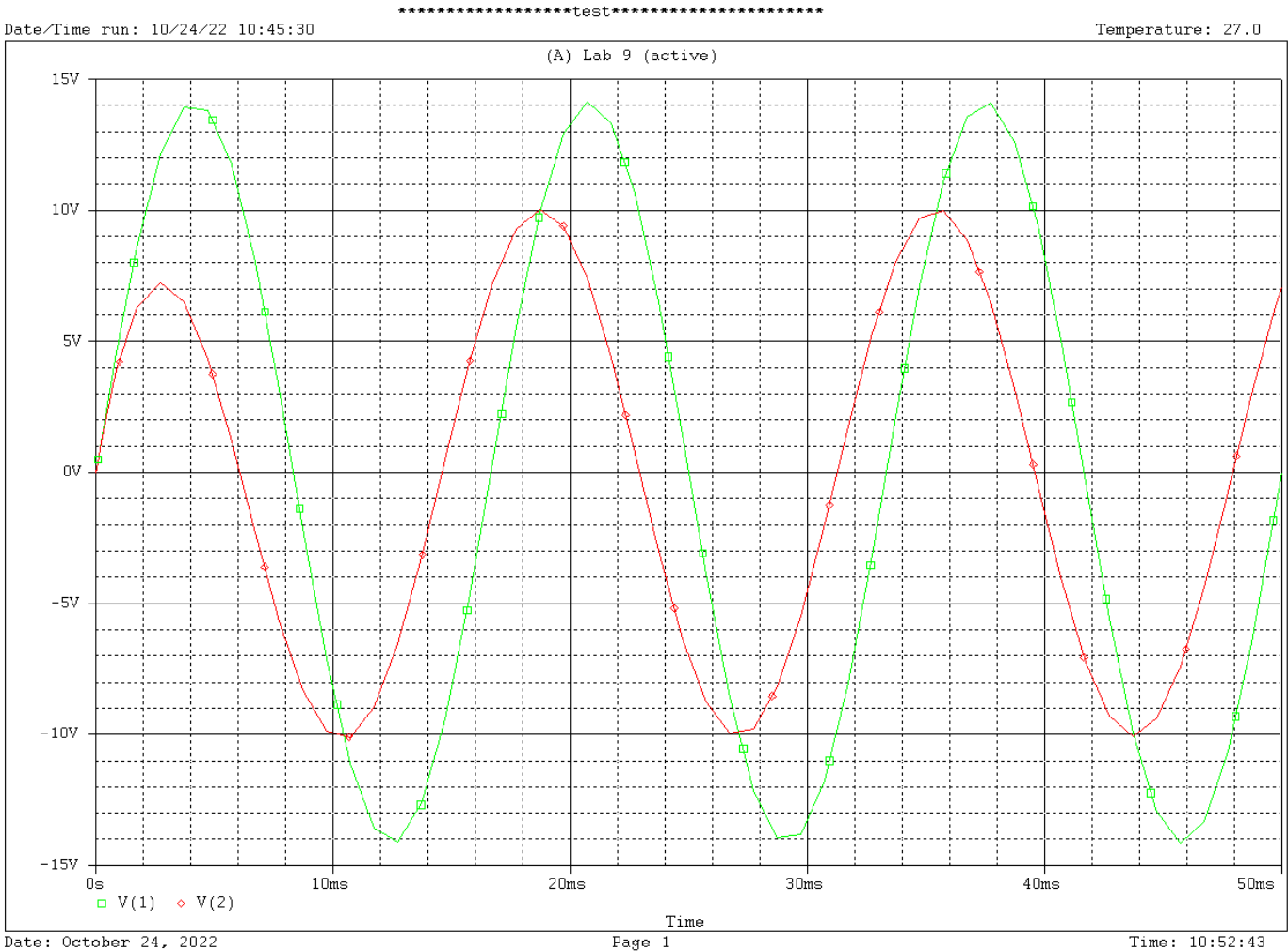


Current traces:

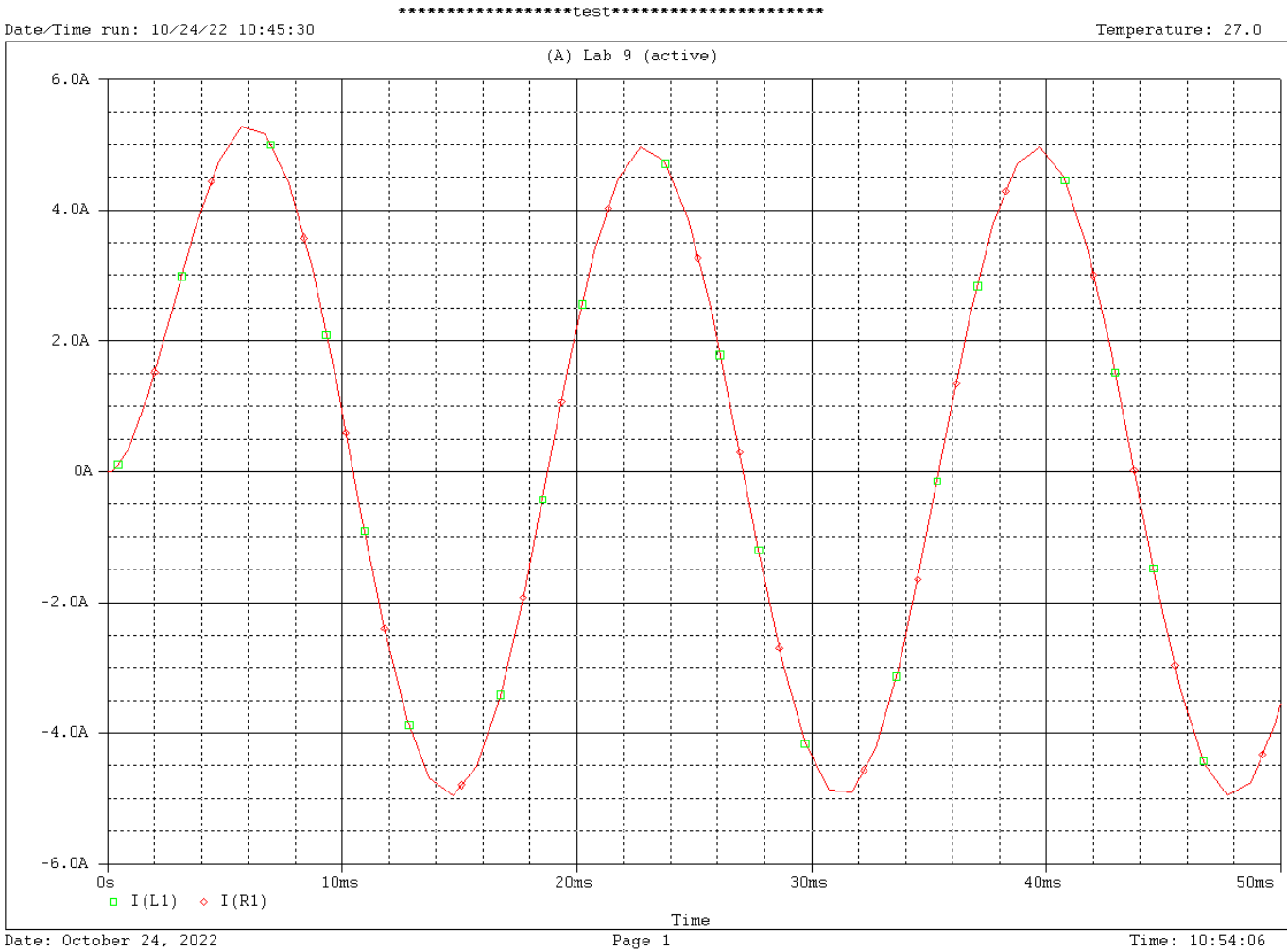

Circuit 2:


Code used

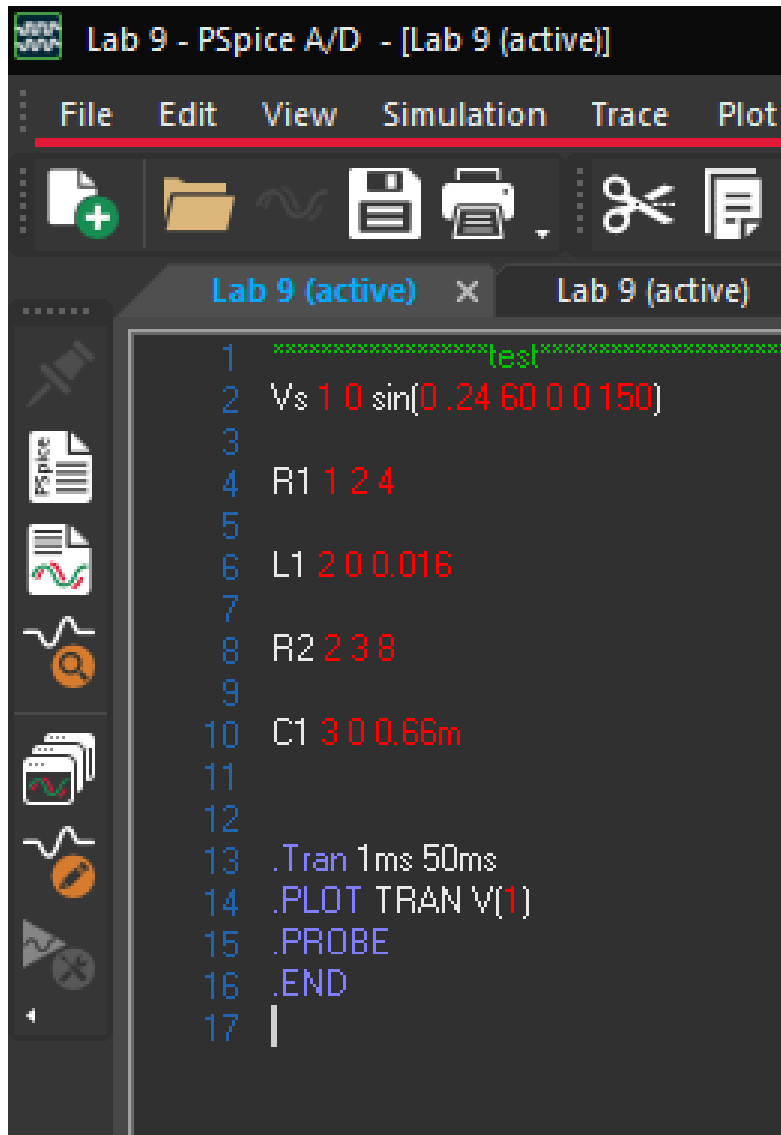


The screenshot shows the PSpice A/D software interface. The title bar reads "Lab 9 - PSpice A/D - [Lab 9 (active)]". The menu bar includes "File", "Edit", "View", "Simulation", "Trace", and "Plot". The toolbar contains icons for creating a new file, opening a file, saving a file, printing, and cutting/copying. The workspace shows a circuit simulation code with the following lines:

```
1 *****test*****
2 Vs 1 0 sin(0 .24 60 0 0 150)
3
4 R1 1 2 4
5
6 L1 2 0 0.016
7
8 R2 2 3 8
9
10 C1 3 0 0.66m
11
12
13 .Tran 1ms 50ms
14 .PLOT TRAN V(1)
15 .PROBE
16 .END
17
```


All traces:

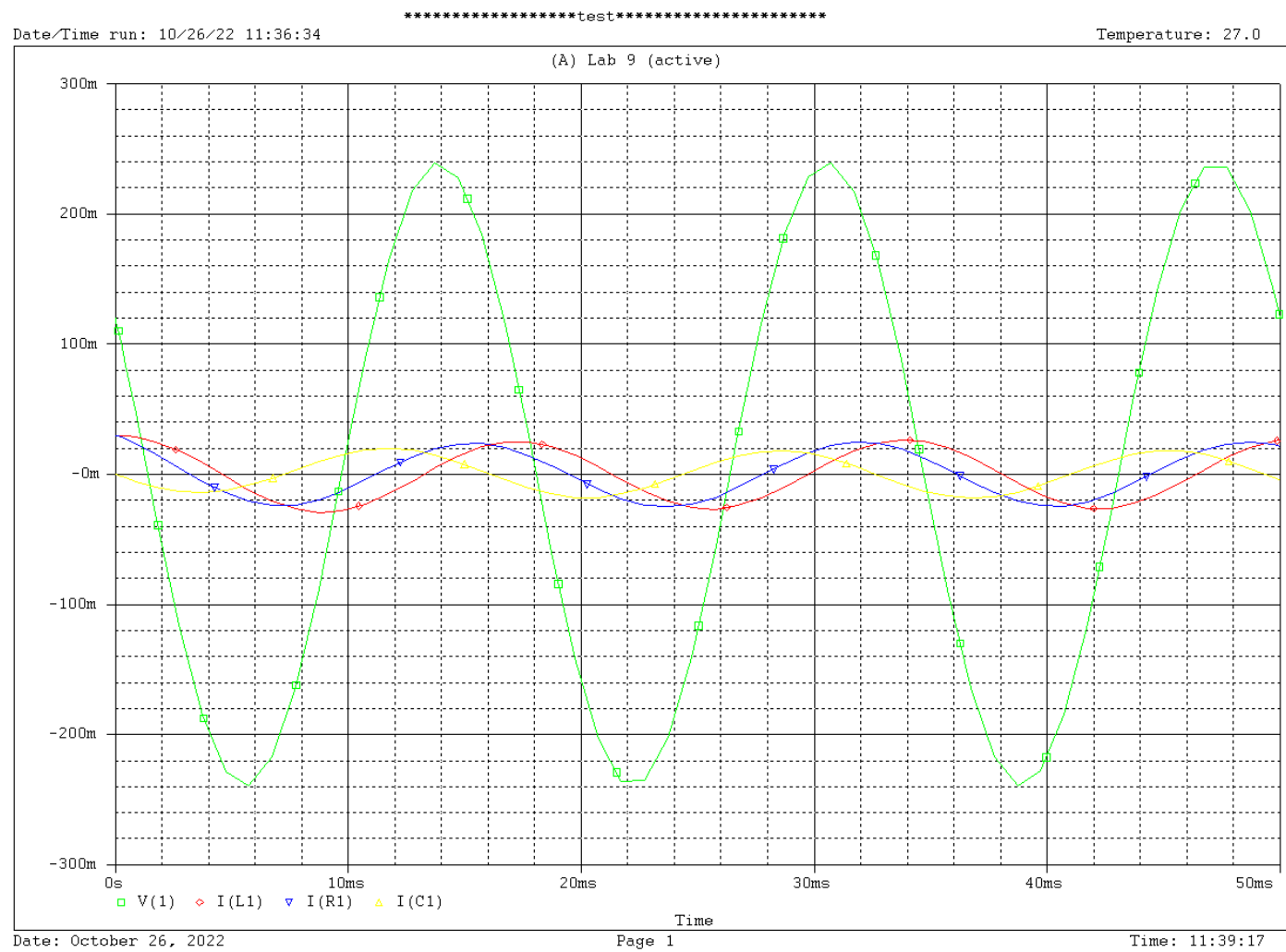

Voltage trace:

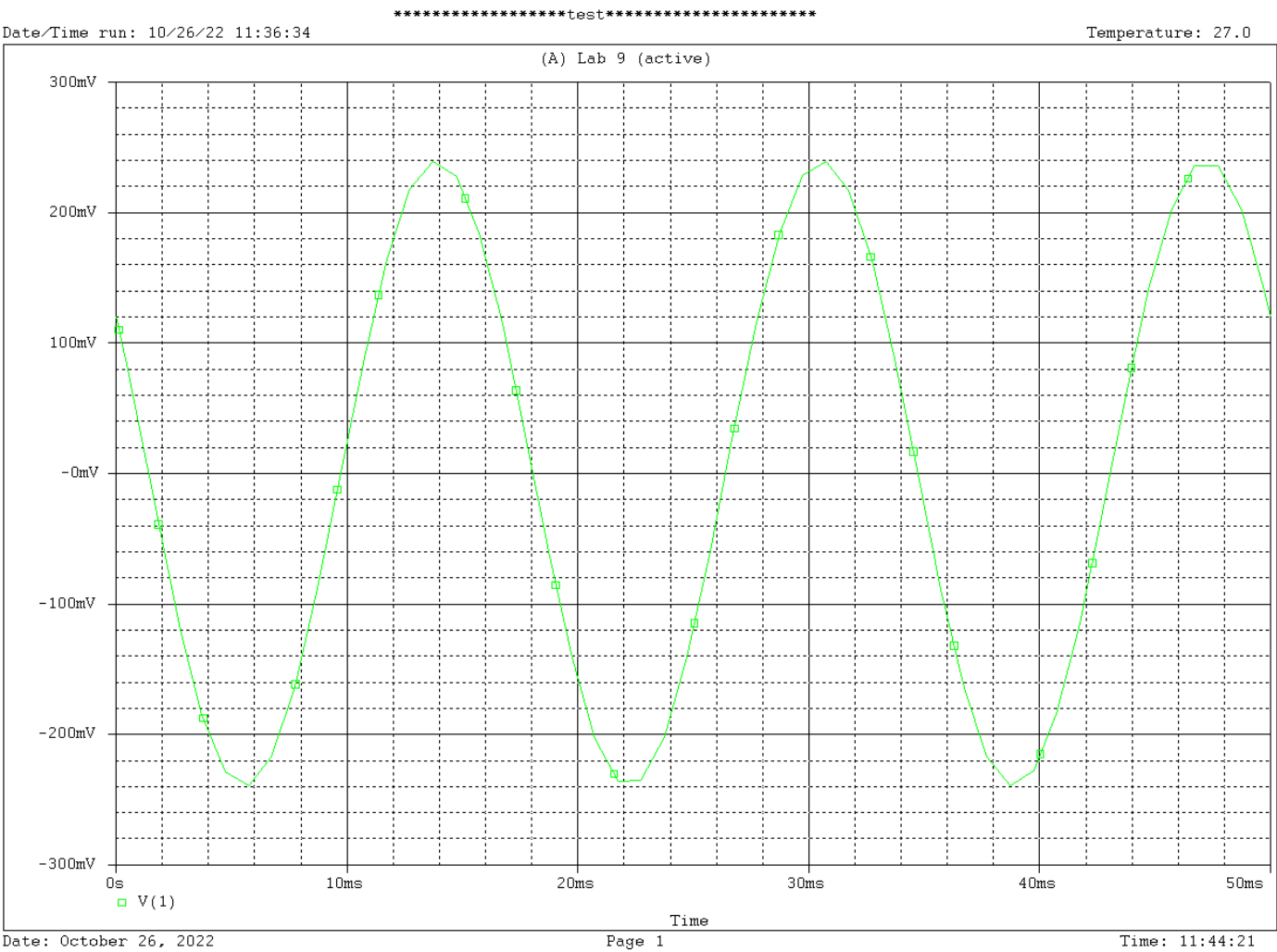

Current traces:

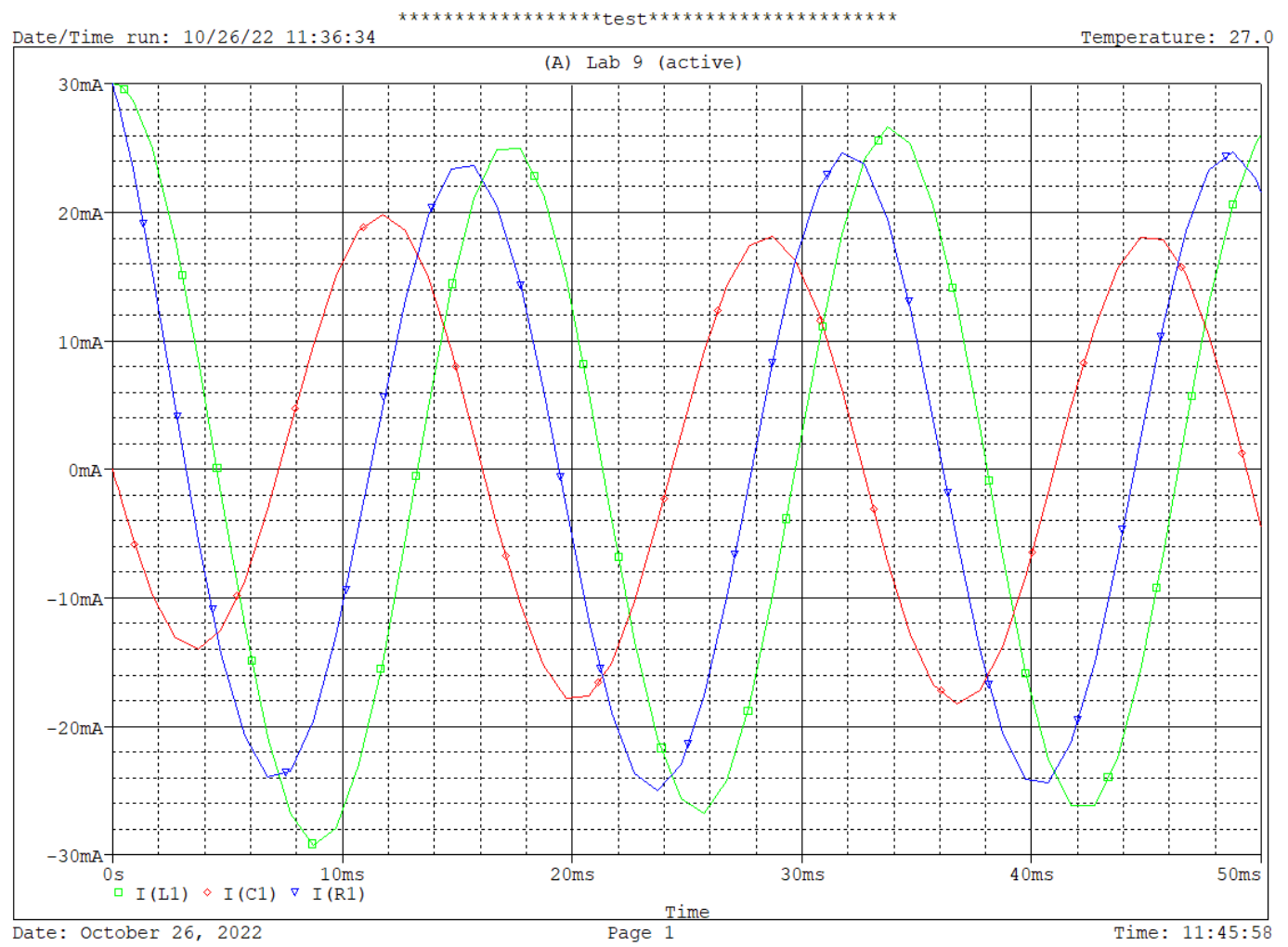

Conclusion

In this lab, I learned how to find the voltage and current as a function of time over two different circuits. After reviewing the answers obtained from handwritten work and pspice, I can conclude the answers concur and are correct.