

Daniel Delgado Acosta

Andrew Goldbaum

Eric Duong


3/24/2022

## Lab 7: Designing a Full-Adder with Verilog

Objective: To build a full adder at the gate level, design and test a full-adder with Verilog.

Provided: TTL7486(1) (XOR), TTL7408 (1) (AND) (1), 7432 (1) (OR), digital trainer kit.


Full Adder Logic Circuit:

 

Full Adder Truth Table:

X	Y	Z	S $x \oplus y \oplus z$	C $xy + ((x \oplus y)z)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Half Adder Screenshot:

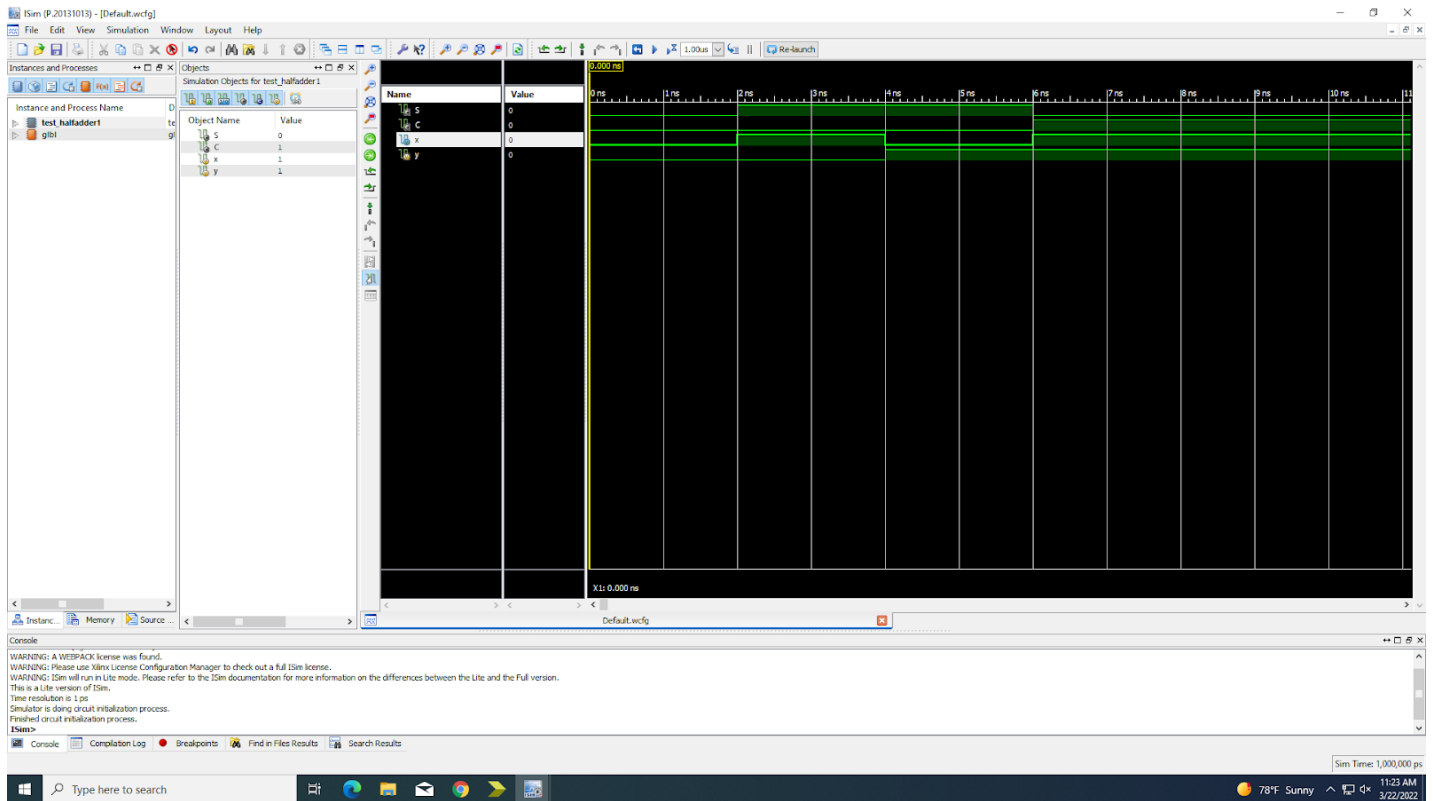

## HalfAdder.v Code:

```
`timescale 1ns / 1ps  
  
/////////////////////////////////////  
/////////////////////////////////////  
  
// Company: CSUSB  
  
// Engineer: Haiyan Qiao, Sean A. Finucane  
  
//  
  
// Create Date: 08:19:36 09/29/2012  
  
// Design Name: Gate-Level Half-Adder (200X)  
  
// Module Name: half_adder  
  
// Project Name: CSE 310 LAB  
  
// Target Devices: NONE  
  
// Tool versions: XILINX ISE (13.4)  
  
// Description:
```

```
//  
// Dependencies:  
//  
// Revision: 1.0 - First Functional Release  
// Revision 0.01 - File Created  
// Additional Comments:  
//  
////////////////////////////////////  
////////////////////////////////////  
module half_adder(  
    input wire x,  
    input wire y,  
    output wire S,  
    output wire C  
);  
  
    assign S = x ^ y;    // XOR Gate  
    assign C = x & y;    // AND Gate  
  
endmodule
```

### Test HalfAdder.v Code:

```
`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

// Company:
// Engineer:
//
// Create Date:    11:12:05 03/22/2022
// Design Name:    half_adder
// Module Name:    C:/Users/006896598/FullAdder1/test_halfadder1.v
// Project Name:    FullAdder1
// Target Device:
// Tool versions:
// Description:
//
// Verilog Test Fixture created by ISE for module: half_adder
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module test_halfadder1;

    // Inputs
    reg x;
```

```

reg y;

// Outputs
wire S;
wire C;

// Instantiate the Unit Under Test (UUT)
half_adder uut (
    .x(x),
    .y(y),
    .S(S),
    .C(C)
);

initial begin
    // Initialize Inputs
    x = 0;
    y = 0;
    #2
    x = 1;
    y = 0;
    #2
    x = 0;
    y = 1;
    #2
    x = 1;
    y = 1;
    #100 ;

    // Wait 100 ns for global reset to finish


```

```
// Add stimulus here
```

```
end
```

```
endmodule
```

## Full Adder Screenshot

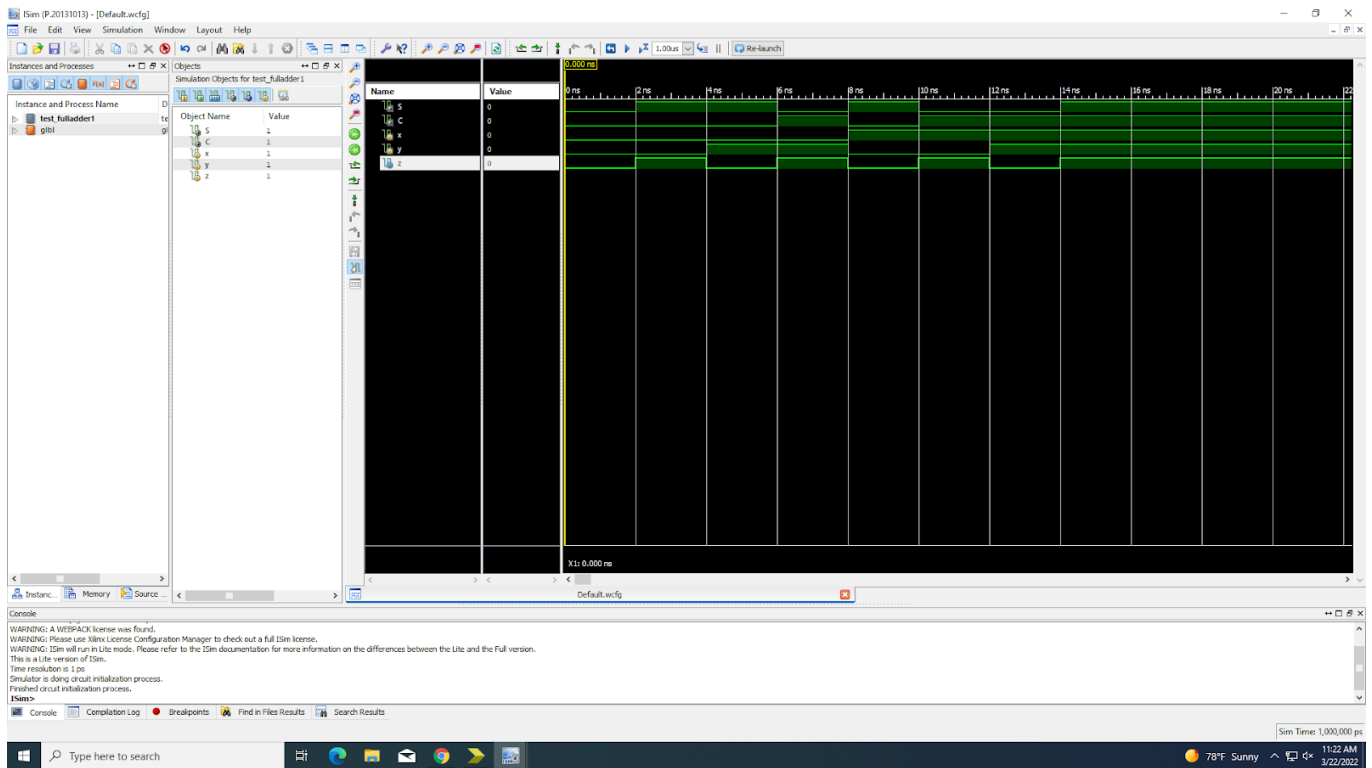

## FullAdder.v Code:

```
`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

// Company: CSUSB

// Engineer: Haiyan Qiao, Sean A. Finucane

//

// Create Date: 08:29:08 09/29/2012

// Design Name: Full-Adder using Half-Adders, Gate-Level (200X)

// Module Name: full_adder

// Project Name: CSE 310 LAB

// Target Devices: NONE

// Tool versions: XILINX ISE (13.4)

// Description:

//
```

```

// Dependencies: half_adder
//
// Revision: 1.0 - First Functional Release
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
////////////////////////////////////
module full_adder(
    input wire x,
    input wire y,
    input wire z,
    output wire S,
    output wire C
);

    // signal interconnects:
    wire S0, C0, C1;

    // internal module declarations (sub-modules):
    half_adder ha_0( .x(x), .y(y), .S(S0), .C(C0) ); // FIRST HALF-
ADDER
    half_adder ha_1( .x(S0), .y(z), .S(S), .C(C1) ); // SECOND
HALF_ADDER

    // output assignments (where still needed):
    assign C = C0 | C1;

endmodule

```



### Test FullAdder.v Code:

```
`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

// Company:
// Engineer:
//
// Create Date:    11:17:06 03/22/2022
// Design Name:    full_adder
// Module Name:    C:/Users/006896598/FullAdder1/test_fulladder1.v
// Project Name:   FullAdder1
// Target Device:
// Tool versions:
// Description:
//
// Verilog Test Fixture created by ISE for module: full_adder
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module test_fulladder1;

    // Inputs
    reg x;
```

```

reg y;
reg z;

// Outputs
wire S;
wire C;

// Instantiate the Unit Under Test (UUT)
full_adder uut (
    .x(x),
    .y(y),
    .z(z),
    .S(S),
    .C(C)
);

initial begin
    // Initialize Inputs
    x = 0;
    y = 0;
    z = 0;

    #2

    x =0;
    y =0;
    z =1;

    #2

    x =0;
    y =1;

```

```
z =0;
```

```
#2
```

```
x =0;
```

```
y =1;
```

```
z =1;
```

```
#2
```

```
x =1;
```

```
y =0;
```

```
z =0;
```

```
#2
```

```
x =1;
```

```
y =0;
```

```
z =1;
```

```
#2
```

```
x =1;
```

```
y =1;
```

```
z =0;
```

```
#2
```

```
x =1;
```

```
y =1;
```

```
z =1;
```

```
#2
```

```
// Wait 100 ns for global reset to finish
```

```
#100;
```

```
// Add stimulus here
```

```
end
```

```
endmodule
```